

ECE115C – Digital Electronic Circuits

Lecture 5: Propagation Delay



Four Key Design Metrics for Digital ICs

◆ Cost of ICs


◆ Reliability



◆ Speed

- Logic delay (today)
- Wire delay (next lecture)

◆ Power

 



$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$



$$\left[|g| > 1 \right]$$

necessary

Performance: Delay Definitions

  

 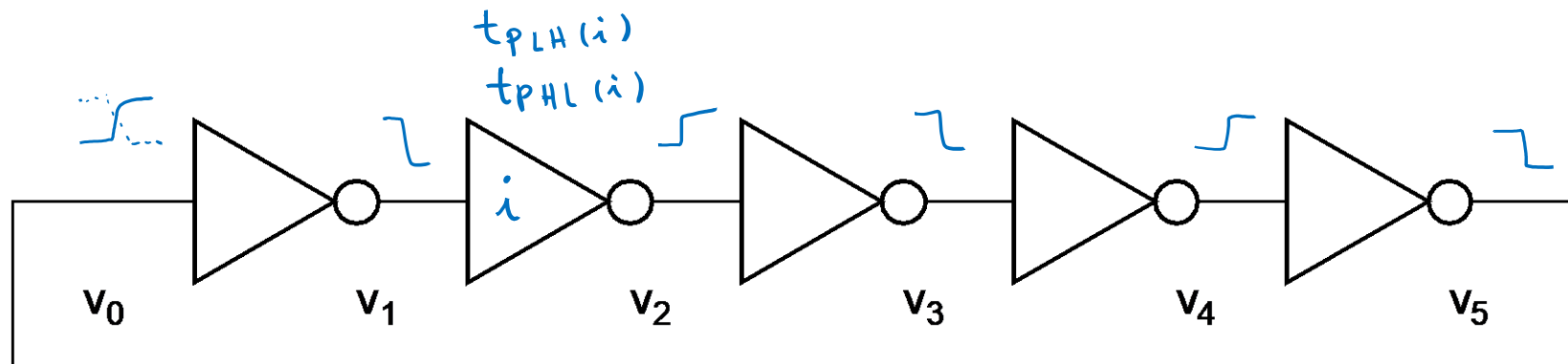Technology Characterization: Ring Oscillator for t_p






measure T by
simulation

$$T = 2 \times t_p \times N$$

Tutorial 2: $t_p = 13ps$

Performance: FO4 Inverter

- Measures quality of design across different technology generations

   


Tutorial 2: $FO4 = 33ps$

CMOS Inverter Propagation Delay: Approach 1

189

MOS Current Model

 

$$t_{pHL} = \frac{C_L \cdot V_{swing}/2}{I_{avg}}$$

out: "1" → "0"

$$t_{pHL} \sim \frac{C_L}{k_n \cdot V_{DD}}$$


reduce delay by:

#1: reduce cap

#2: increase $\frac{w}{L}$
(factors into C_L)

#3: increase voltage

A First-Order RC Network: Step Response

 

Step response:

$$v_{out}(t) = (1 - e^{-t/\tau}) \cdot v_{in}$$

① $v_{out}(0) = V_0$

② $v_{out}(\infty) = V_{\infty}$ $V_0, V_{\infty} \in \{V_{OL}, V_{OH}\}$

Switching pt: $v_{out}(t_{p_{HL}}) = V_M$

$\tau = RC$

$t = \infty: e^{-t/\tau} = 0$

②

GENERAL FORMULA


$$v_{out}(t) = V_{\infty} + (V_0 - V_{\infty})e^{-t/\tau}$$

① $t = 0: e^{-t/\tau} = 1$

special case: $V_{\infty} = V_{DD}$ & $V_0 = 0$

$\hookrightarrow v_{out}(t) = V_{DD}(1 - e^{-t/\tau})$

 A First-Order RC Network: Propagation Delay



Propagation delay:

$$t_p = \tau \cdot \ln 2 = 0.69RC$$

$$t_s \sim 2.2 RC \quad \text{slope 90\% point}$$

$$V_{out}(t) = V_{\infty} + (V_0 - V_{\infty}) e^{-t/\tau}$$

$$V_{out}(t_p) = V_M$$

$$V_M = V_{\infty} + (V_0 - V_{\infty}) e^{-t_p/\tau}$$

$$t_p = \tau \ln \frac{V_0 - V_{\infty}}{V_M - V_{\infty}}$$

GENERAL

special case:


$$V_M = \frac{V_{DD}}{2}$$

$$V_0 = 0, V_{\infty} = V_{DD}$$


$$t_p = \tau \ln \frac{-V_{DD}}{-V_{DD}/2} = \tau \ln 2 = 0.69 RC$$

CMOS Inverter Propagation Delay: Approach 2

MOS Resistance Model

 


Review: Transistor as a Switch

 

$$R_{on} \approx \frac{1}{2} (R_0 + R_{mid})$$

 
↑
good approximation (I - $V \approx$ linear)



$$R_{on} = \frac{1}{2} \left(\frac{V_{DD}}{I_{DSAT} \cdot (1 + \lambda V_{DD})} + \frac{V_{DD}/2}{I_{DSAT} \cdot (1 + \lambda V_{DD}/2)} \right)$$

$$R_{on} \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{5}{6} \lambda V_{DD} \right)$$


Transient Response

 

Design for Performance

- ◆ Keep capacitances small
- ◆ Increase transistor sizes
 - watch out for self-loading!
- ◆ Increase V_{DD} (?)
 
$$t_{pHL} \sim \frac{C_L}{k_n \cdot V_{DD}}$$




$$R_{on} \sim \frac{1}{w}$$

$$C_p, C_g \sim w$$



$$R_{on} \cdot C_p \sim \frac{1}{w} \cdot w = \underline{\underline{\text{constant}}}$$

Delay as a function of V_{DD}

189

 

Device Sizing

 
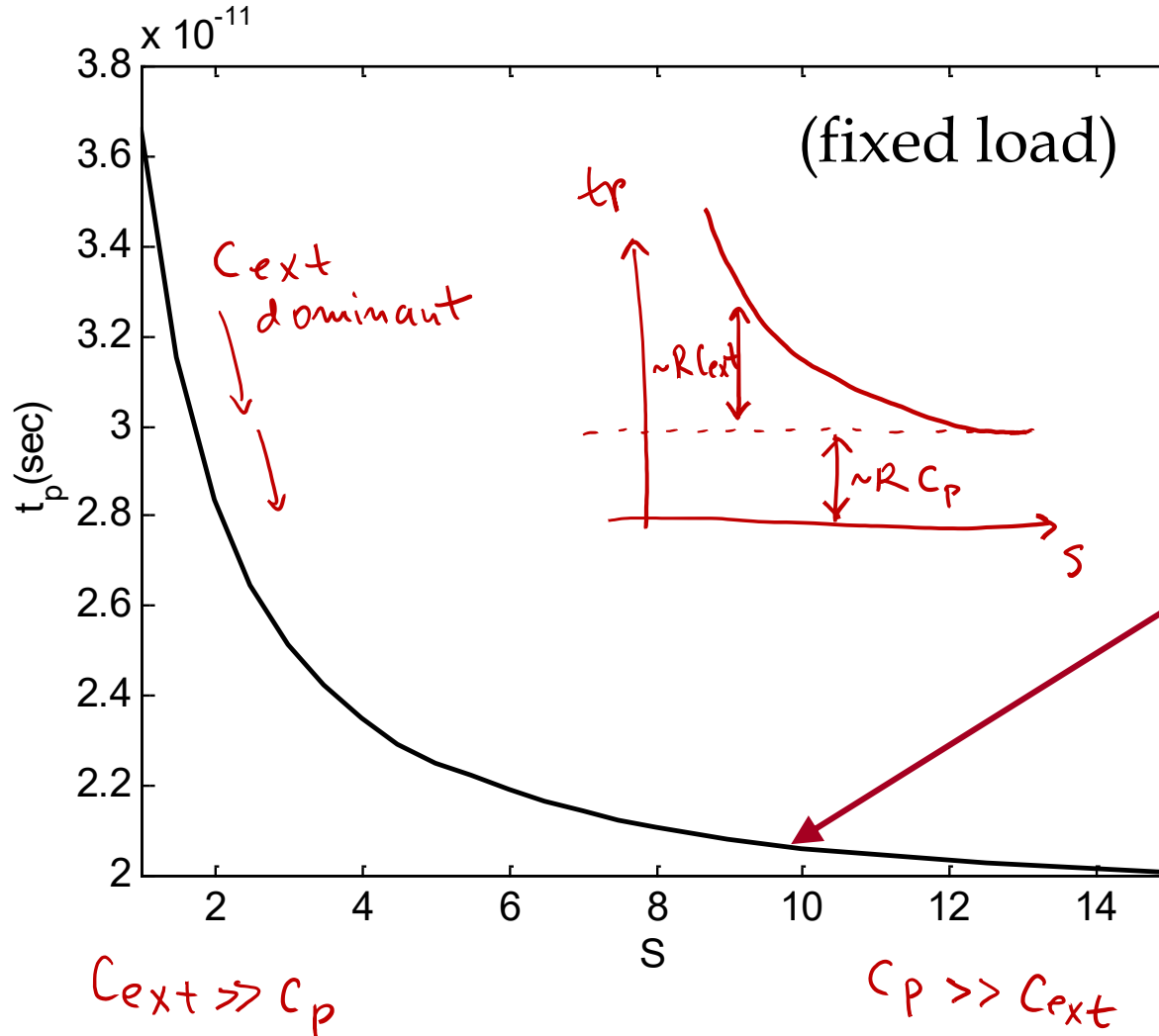


**Self-loading effect:
Intrinsic capacitances
dominate**

Handwritten red notes:

- $W \rightarrow S \cdot W \uparrow$
- $R \sim \frac{1}{S} \downarrow$
- $C_p \sim S \uparrow$

NMOS/PMOS Ratio

  


$$\beta = W_p / W_n$$

typical std-cell lib:

$$\frac{W_p}{W_n} \approx 1.3 - 1.7$$

Impact of Rise Time on Delay

 


$$t_p = \underline{t_{step(i)}} + \eta \cdot t_{step(i-1)}$$


$$t_p \sim 0.69 RC$$

$$t_s \sim 2.2 RC$$


Two Inverters

 


$t_p = ?$

 


Computing the Capacitances

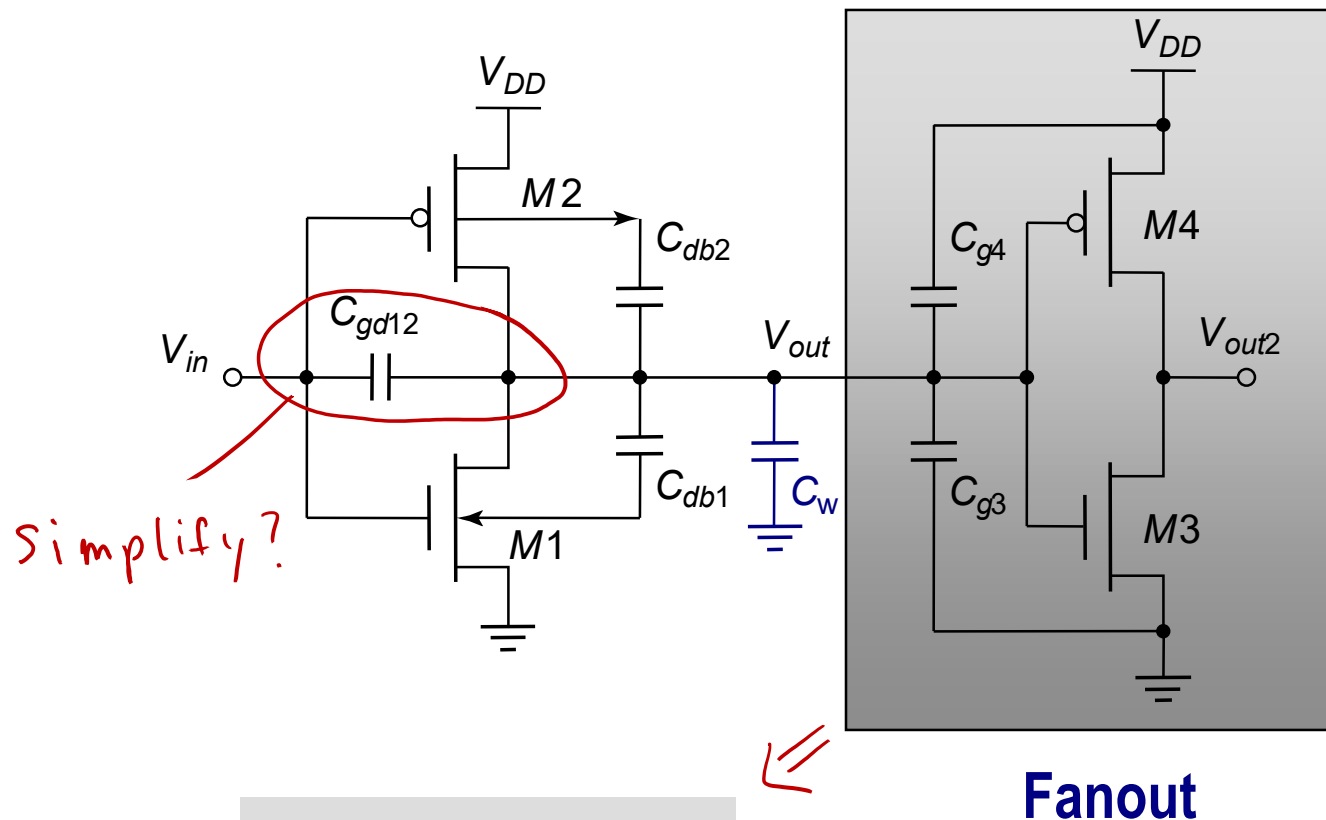

**Simplified
Model**

 

The Miller Effect

 

“A capacitor experiencing identical but opposite voltage swing at both terminals can be replaced by a capacitor to ground, whose value is two times the original value”

Miller Effect


$$i_1 = \frac{V_{in}(1 - A)}{Z_F}$$

↓


$$Z_1 = \frac{Z_F}{1 - A}$$

↑

$$i_1 = \frac{V_{in}}{Z_1}$$

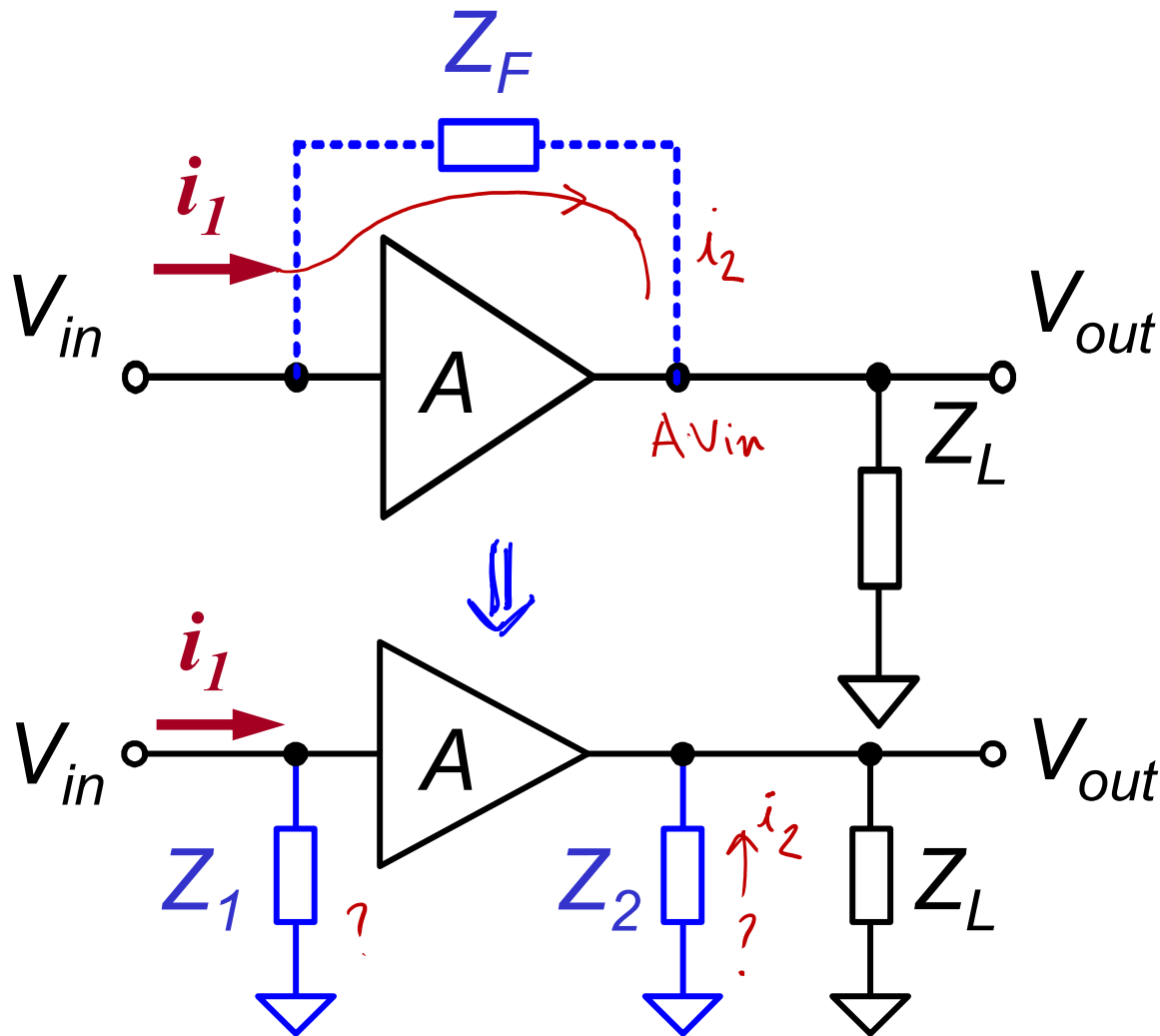


Miller Effect

 

$$Z \sim \frac{1}{j\omega C}$$

$$Z_1 = \frac{Z_F}{1 - A}$$


$$C_1 = C_F \cdot (1 - A)$$

 


$$Z_2 = \frac{Z_F}{1 - \frac{1}{A}}$$

$$C_2 = C_F \cdot (1 - 1/A)$$

The CMOS Inverter: C_{in}

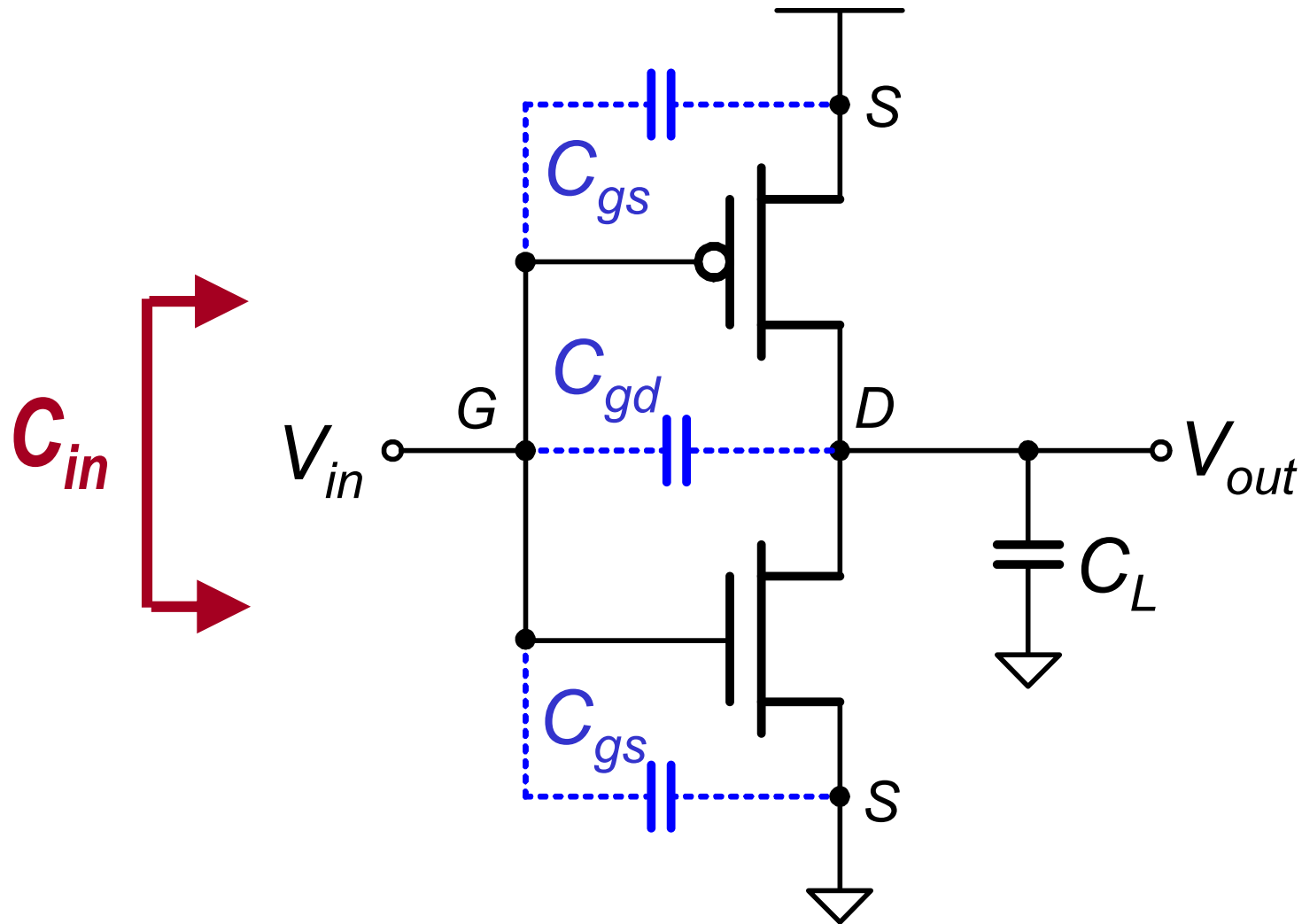

CMOS Inverter Example: C_{in}

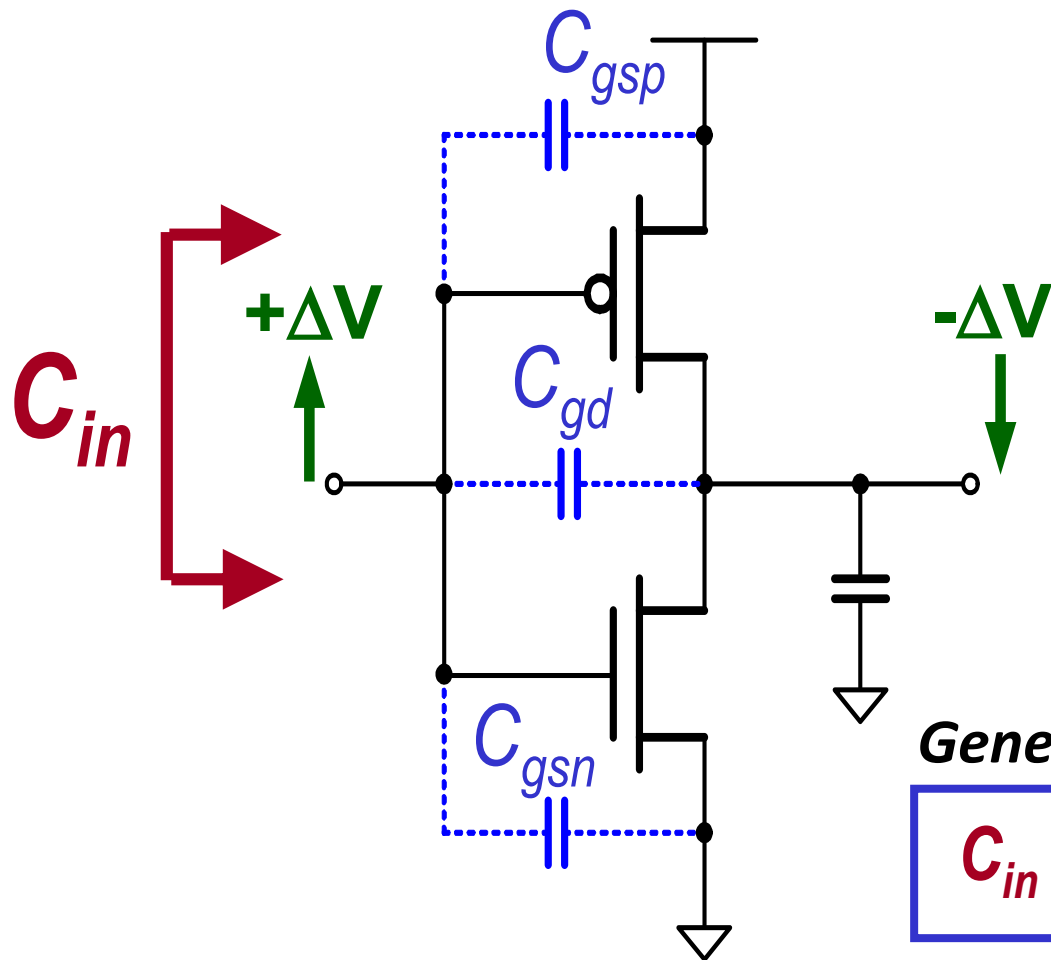

$$C_{gs} = C_{gsn} + C_{gsp}$$

$$C_{gd} = C_{gdn} + C_{gdp}$$



$$A = -1$$

General formula:


$$C_{in} = C_{gs} + C_{gd}$$

Approximation for CMOS gates: $C_{in} = C_{gs} + C_{gd}$

Computing the Capacitances

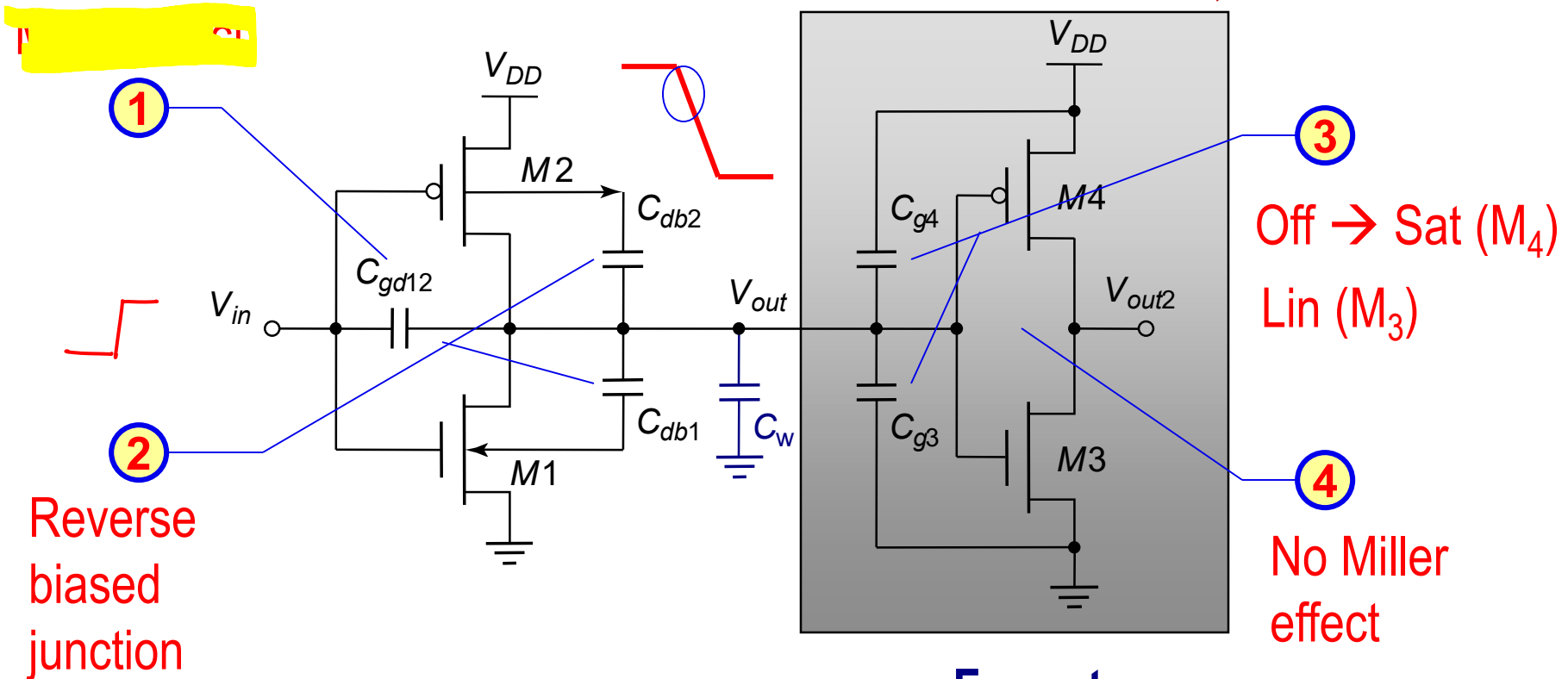 

Simplified Model

 

Fanout

$$C_{ext} = C_w + C_{g3} + C_{g4} + C_{db1} + C_{db2} + 2(C_{gd1} + C_{gd2})$$

C_{par}

Miller factor \rightarrow


Computing the Capacitances

- ② Reverse biased junction
- ① Miller effect

Capacitor	Expression
C_{gd1}	$CGD0 \cdot W_n$
C_{gd2}	$CGD0 \cdot W_p$
C_{db1}	$K_{eqn} (AD_n \cdot CJ + PD_n \cdot CJSW)$
C_{db2}	$K_{eqp} (AD_p \cdot CJ + PD_p \cdot CJSW)$
C_{g3}	$C_{ox} \cdot W_n \cdot L_n$ (Off \rightarrow Sat*)
C_{g4}	$C_{ox} \cdot W_p \cdot L_p$ (Lin*)
C_w	From Extraction
C_L	Σ

* assuming LH transition at V_{out}

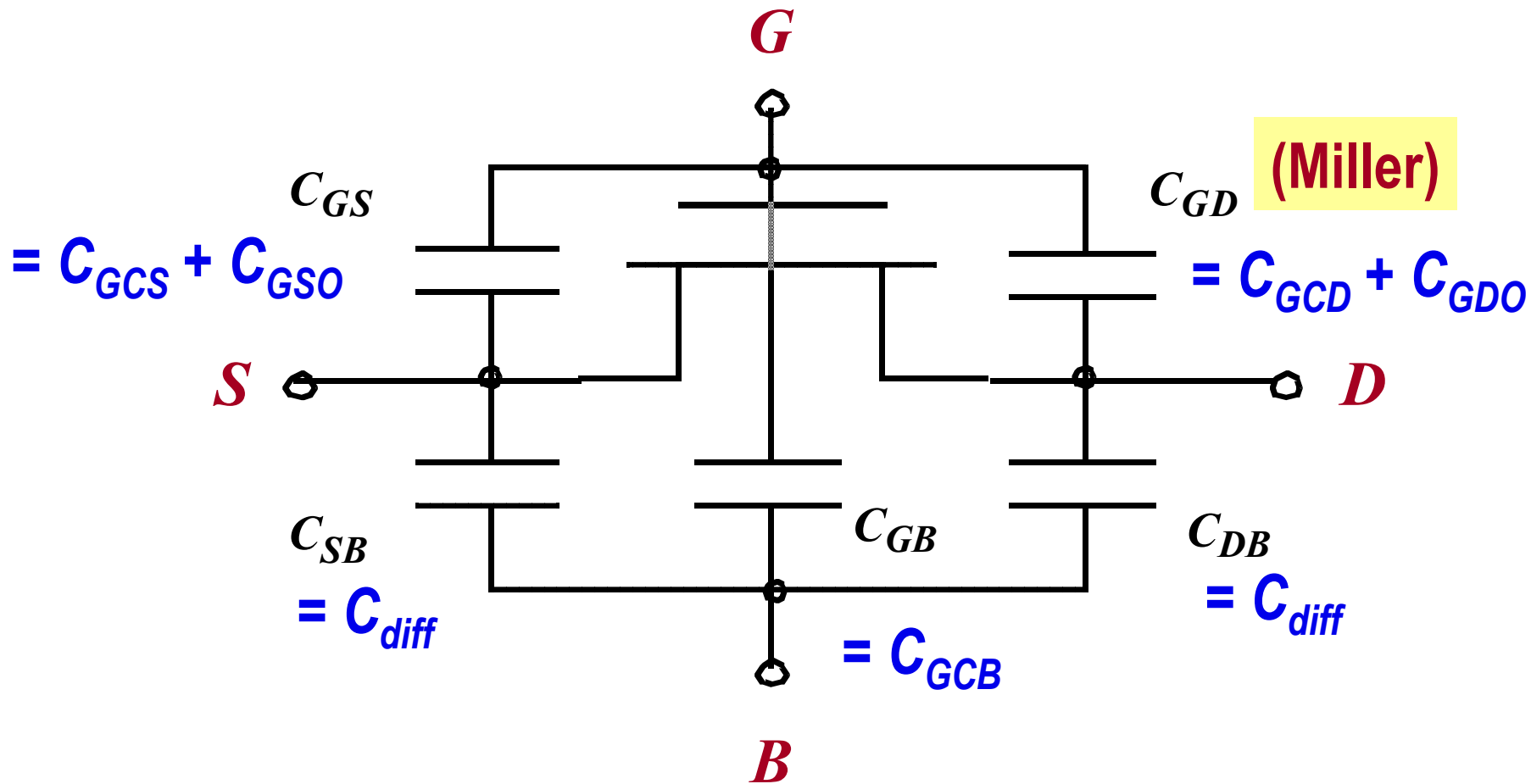Capacitive Device Model For Circuit Analysis



Simplified Macro Model

- ◆ **Consider two macro capacitances**
 - Input gate capacitance, C_{in} (or C_{gate})
 - Output parasitic (self-loading capacitance), C_{par}
- ◆ **Assume that both capacitances are linearized**
 - C_{in} and C_{par} are proportional to W
(remember, we keep L at L_{min} , so it is lumped into constant)
 - In our 90nm technology, C_{par} / C_{in} is about 0.6
- ◆ **For gate delay analysis, we will use:**

$$C_{in} = 2fF/\mu m$$

$$C_{par}/C_{in} = 0.61$$