

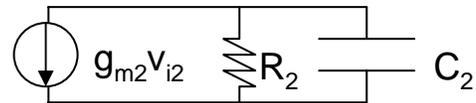
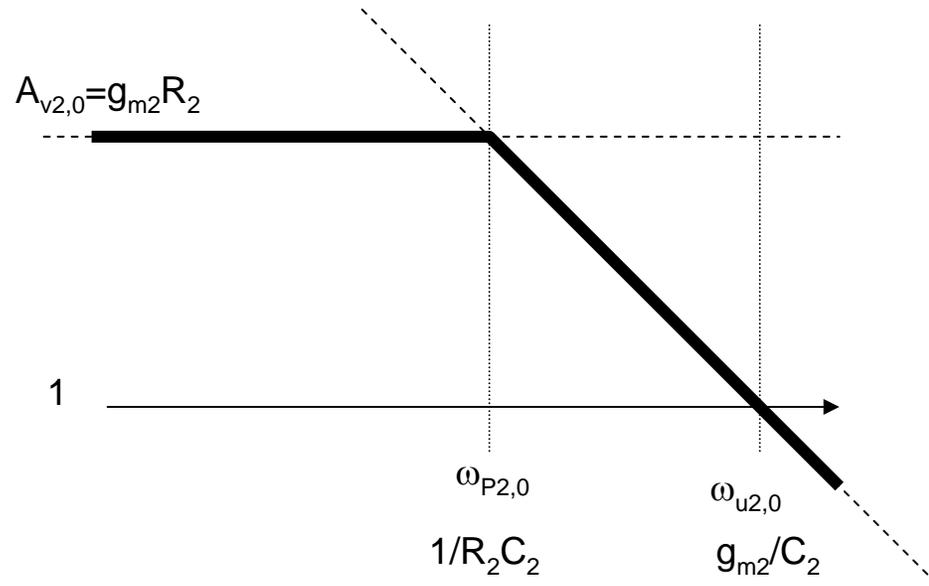
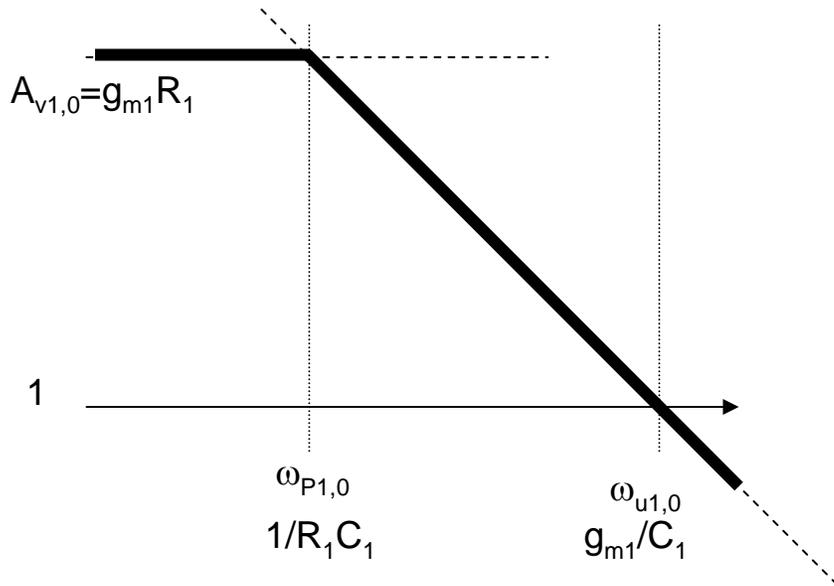


1st and 2nd stage gain with $C_c=0$

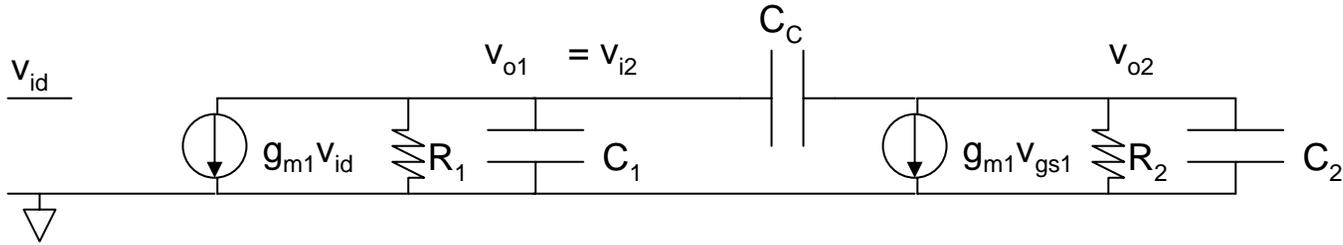

Overall gain with $C_c=0$

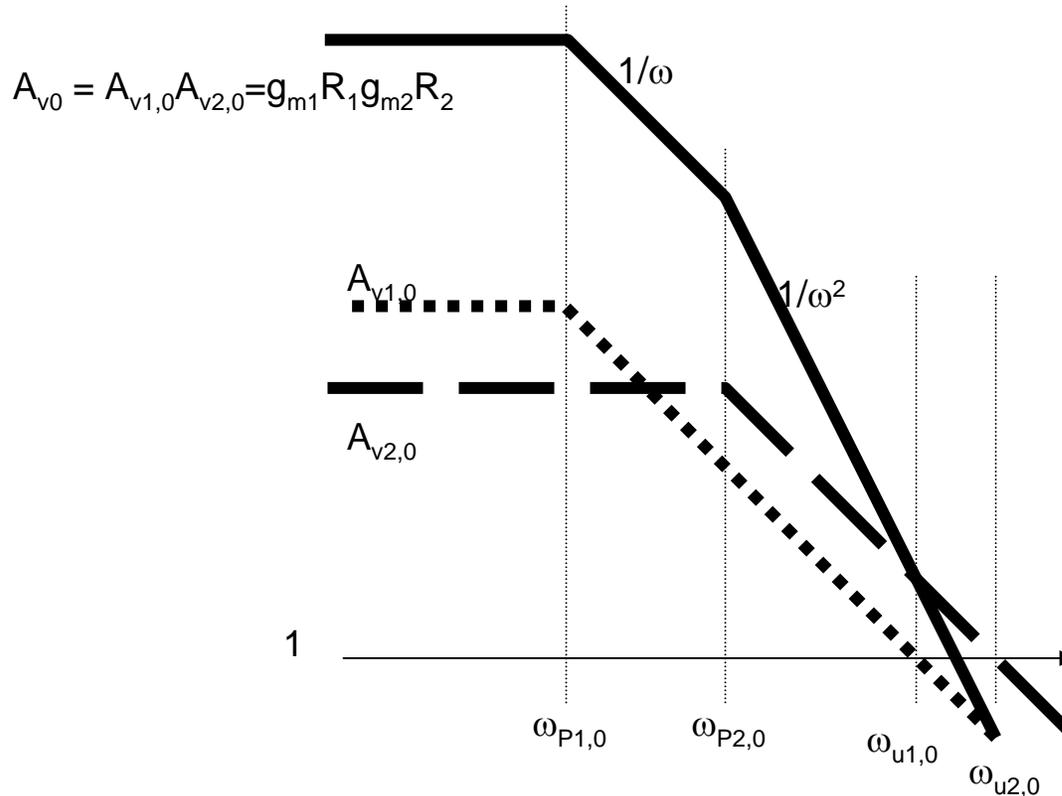

Things to think about:

1. What is the equation for gain between the first two poles?
2. What is the equation for gain after the second pole?
3. What is the gain at the first-stage unity gain frequency?
4. What is the gain at the second-stage unity gain frequency?
5. What is the unity gain frequency?

Example with $C_C=0$

$$g_{m1} = 1\text{mS}$$

$$R_1 = 100\text{k}$$

$$C1 = 10\text{pF}$$

$$g_{m2} = 10\text{mS}$$

$$R_2 = 1\text{k}$$

$$C2 = 10\text{pF}$$

$$A_{v1,0} = 100$$

$$\omega_{p1} = 1\text{M}$$

$$\omega_{u1} = 100\text{M}$$

$$A_{v2,0} = 10$$

$$\omega_{p2} = 100\text{M}$$

$$\omega_{u2} = 1\text{G}$$


$$A_{v0} = 1000$$

$$A_{v1,0} = 100$$



$$A_{v2,0} = 10$$

What's the phase margin?
 What's the phase margin if I use
 this amplifier with $f=0.1$?

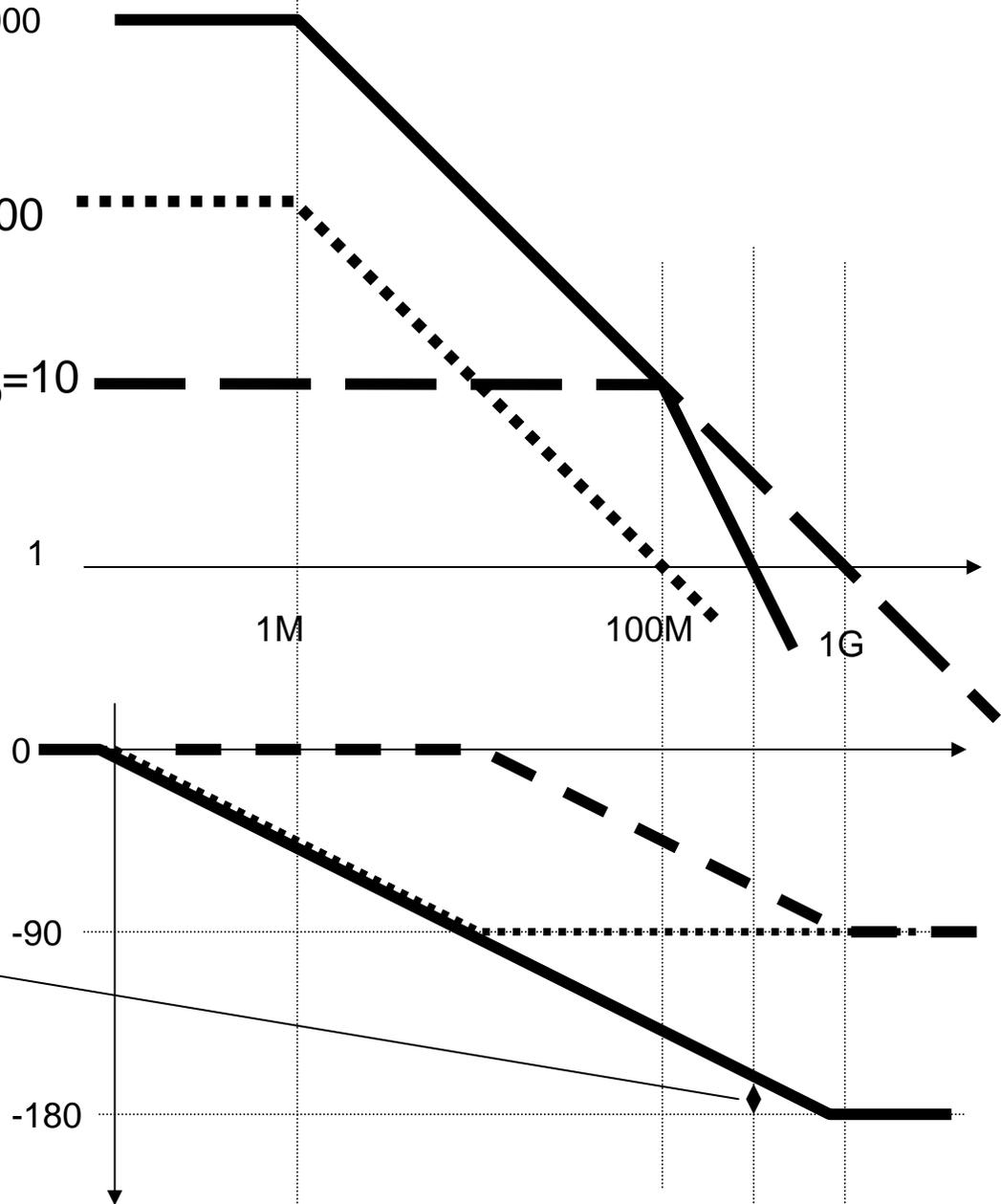
Phase margin
 for unity gain ($f=1$)
 feedback



Z_{o1} with $A_{v2,0} C_C > C_1 > C_C$

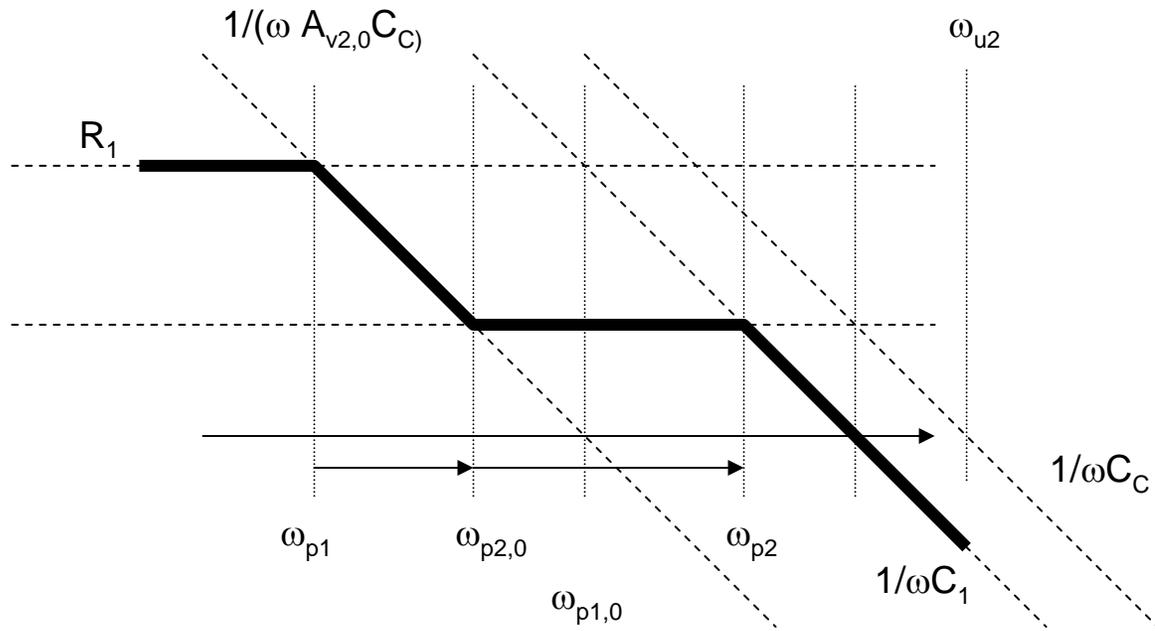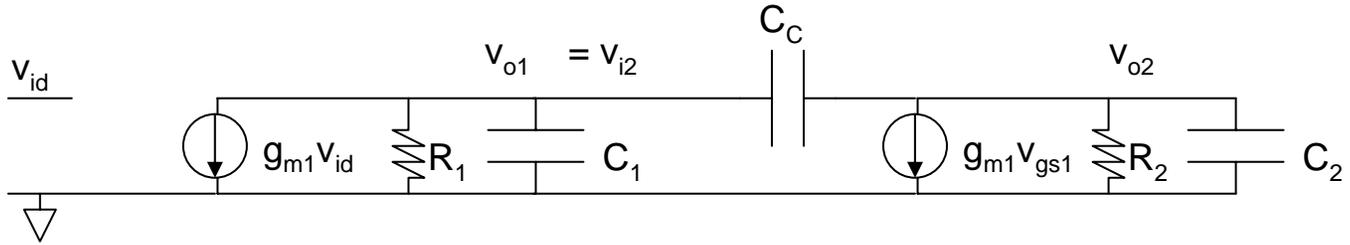

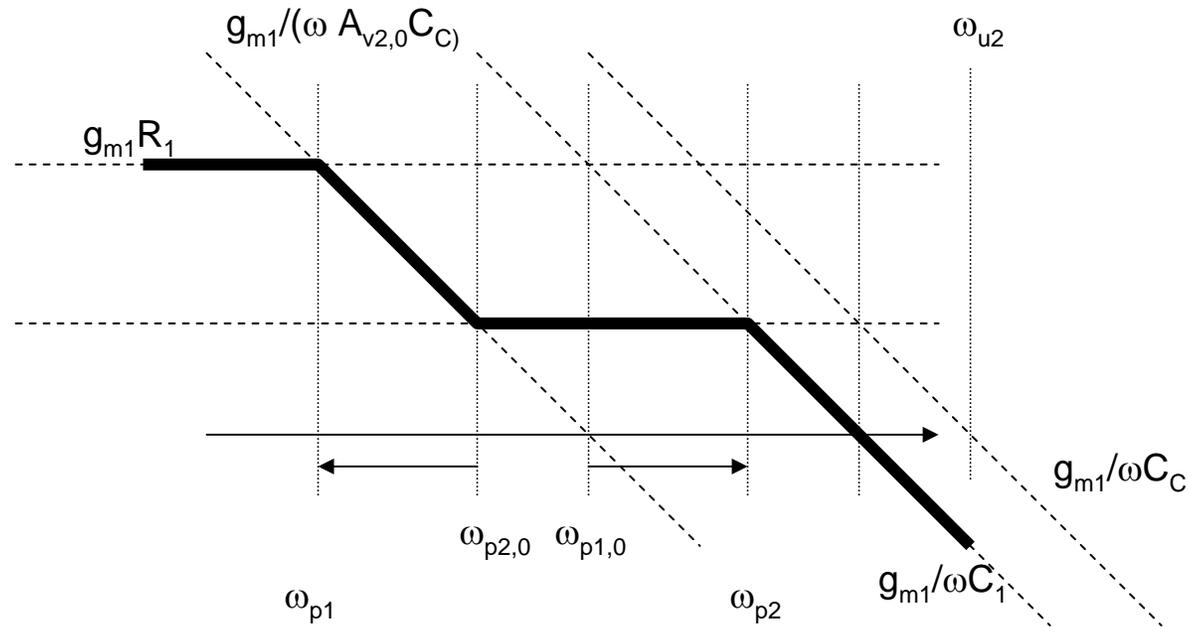
$$A_{v1} = g_{m1} Z_{o1} \text{ with } A_{v2,0} C_c > C_1 > C_c$$



Things to think about:

1. What's the equation for the gain in the various sections?
2. What does the curve look like if $C_c > C_1$?
3. What does the curve look like if $\omega_{p2,0} > \omega_{p1,0}$?
4. What is the frequency ratio of the old and new first pole?
5. What is the frequency ratio of the old and new second pole?
6. Answer questions 4 & 5 assuming 2 and/or 3.

Overall gain with $C_1 > C_c > 0$

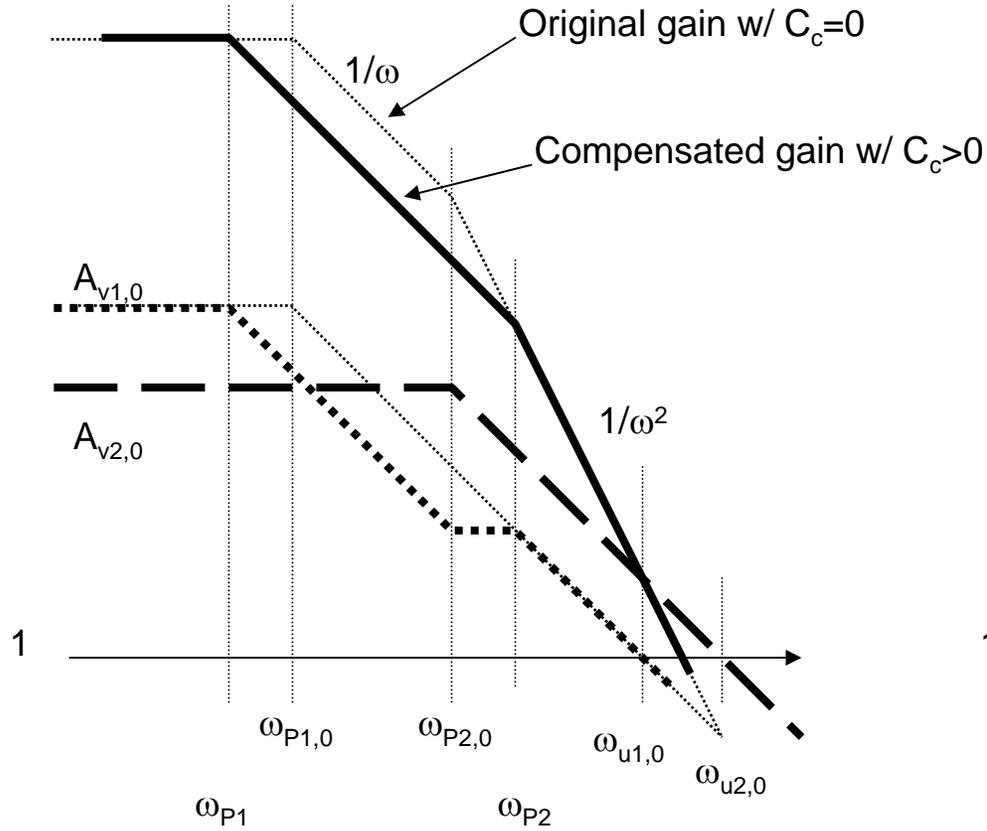

Overall gain with $\omega_{p2} > \omega_u$

